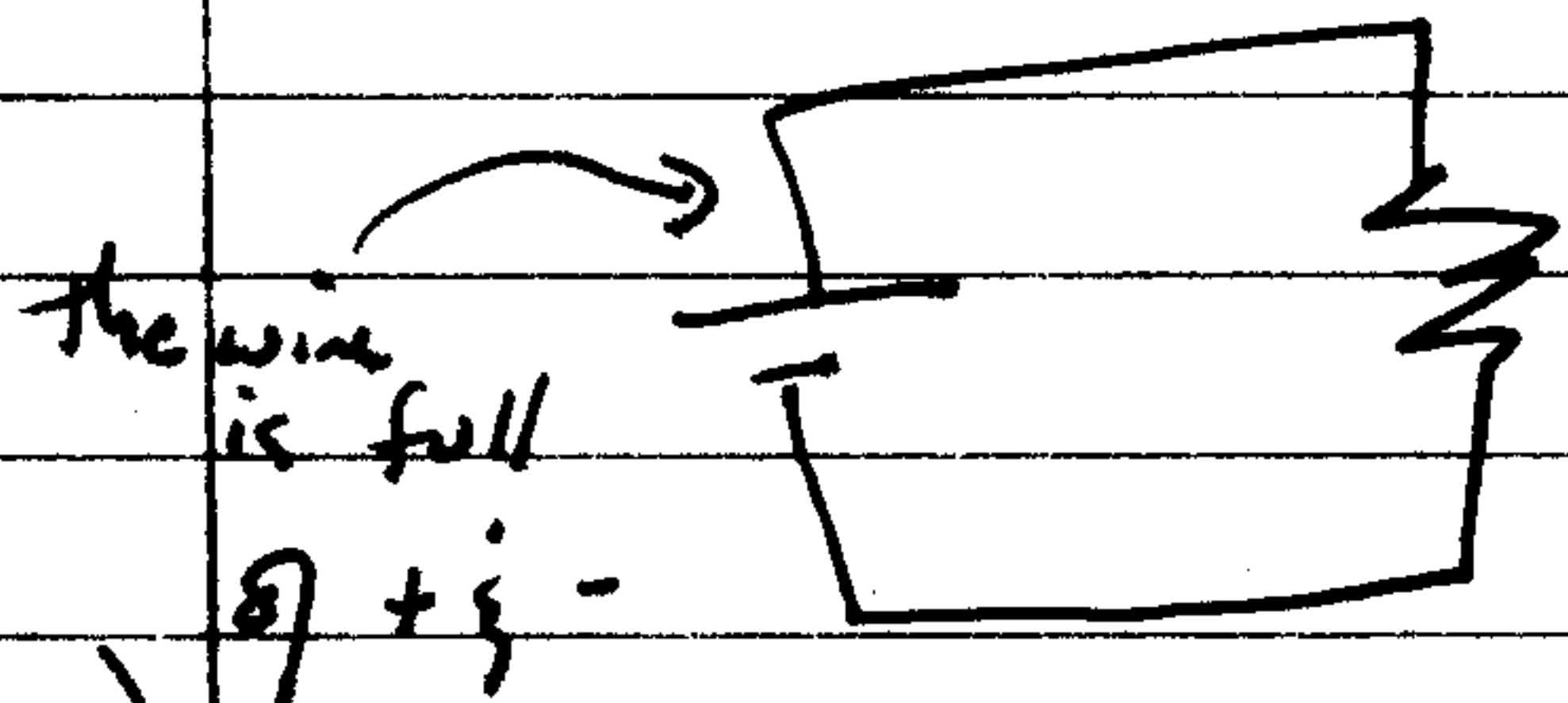


Exam #2


1) An electric current is a flow of charged particles



a) charges, the current is the ~~moving~~ ^{average} movement of the charged ptcls that are free to move.

b) The battery provides the oomph but without the path for the ptcls to move along & a wealth of pre existing charged ptcls in the wire & resistor no current would flow.

2 This circuit can be thought of as

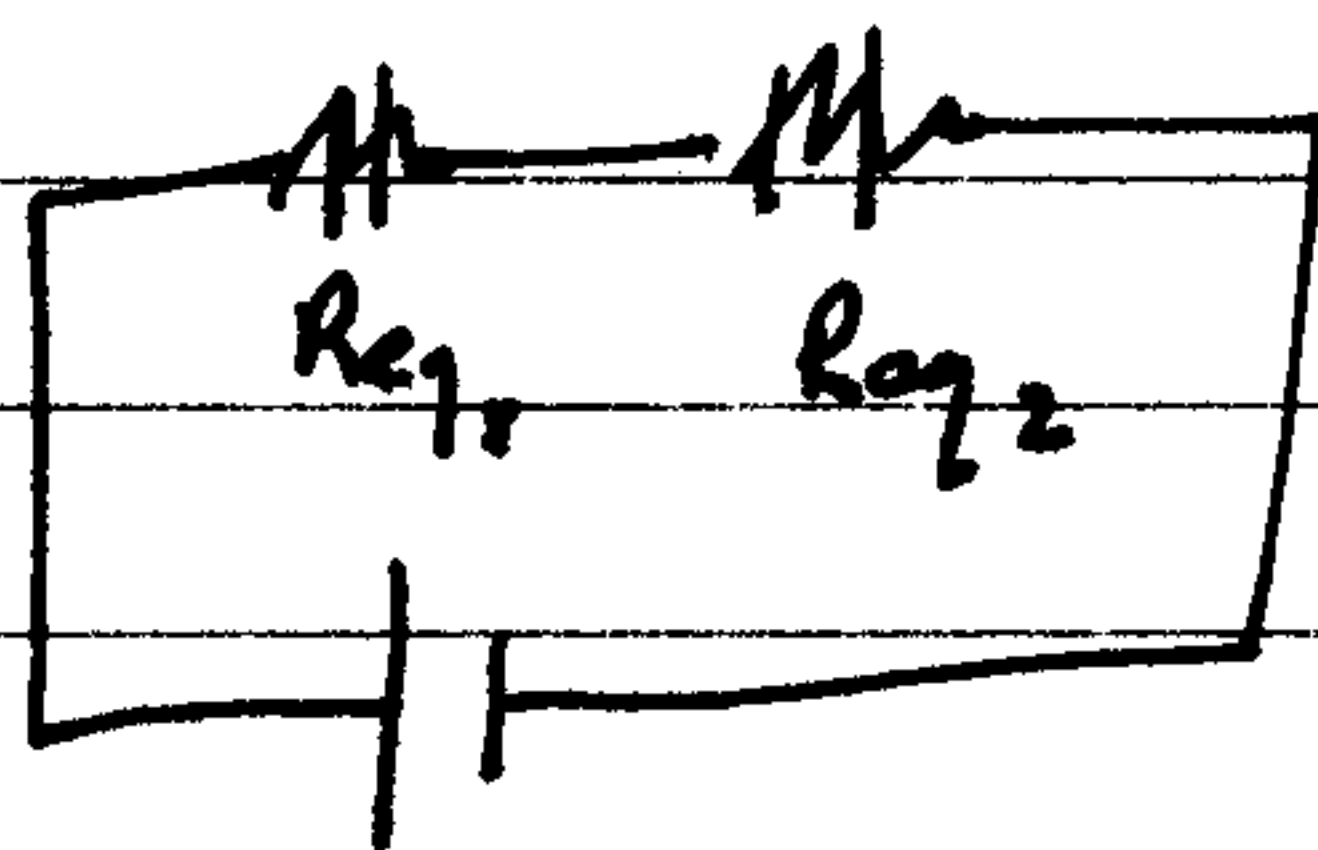

parallel resistors

$$\frac{1}{R_{eq1}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R}$$


$$= \frac{4}{R}$$

$$R_{eq1} = 25\Omega$$

and

$$\frac{1}{R_{eq2}} = \frac{1}{R} + \frac{1}{R}$$

$$\Rightarrow R_{eq2} = \frac{R}{2}$$

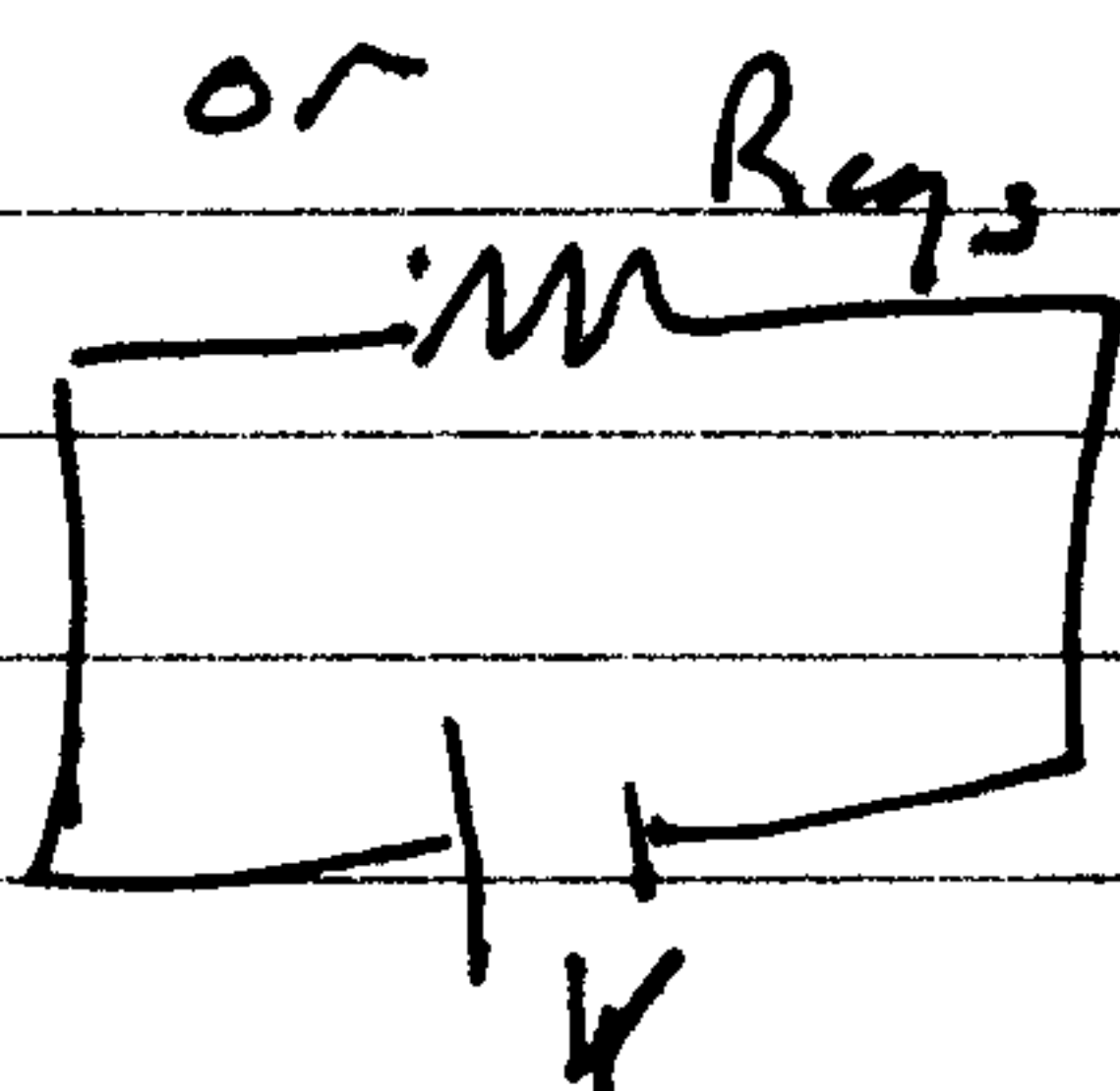

series resistors


$$R_{eq3} = R_{eq1} + R_{eq2}$$

$$= \frac{3R}{4} = 75\Omega$$


Since $V = iR$

$$i = \frac{V}{R} = \frac{12V}{75\Omega} = 0.16A$$

3)

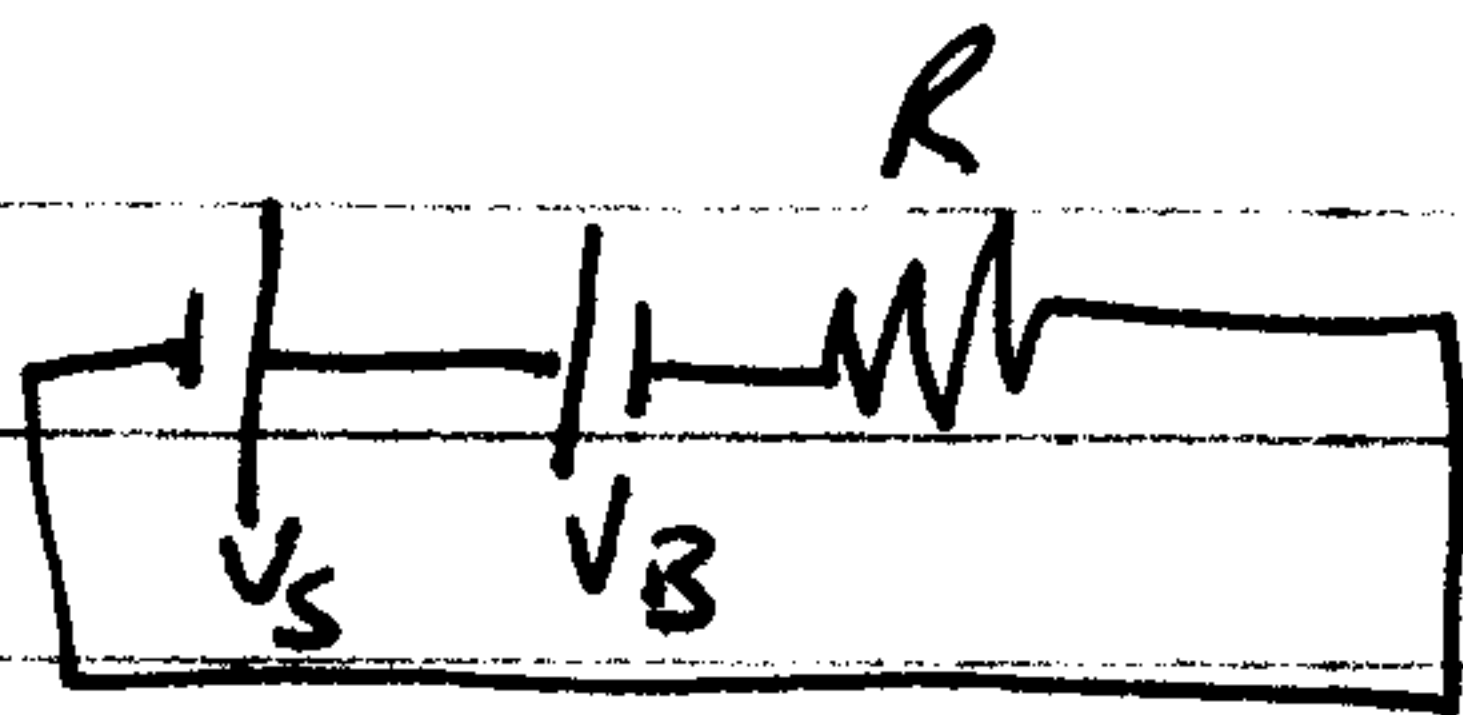

is equivalent to

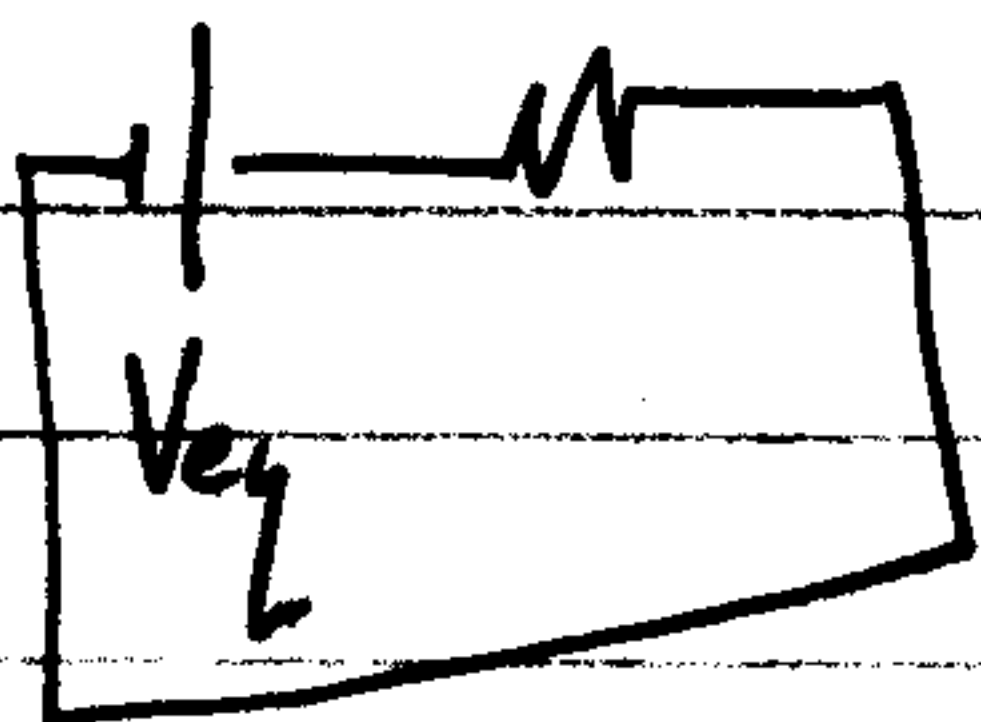

$$V_{eq} = V_S - V_B = 0.8V$$

a) so $i = V/R = \frac{0.8V}{2\Omega} = 0.4A$

b) The rate at which ~~power~~ Energy is being stored is

$$i V_B = 0.4A \times 4.5V = 1.8W$$

c) The rest of the power supplied by the charger is lost to heat

$$i V_R = 0.4A (0.8V) = 0.32W$$

d) If the battery can store 3kJ of energy it will take

$$P t = \text{Energy} = E$$


$$t = E/P = 3000J / 1.8W = 1667s$$

$$\approx 28 \text{ min}$$

$$\approx 1/2 \text{ hr.}$$

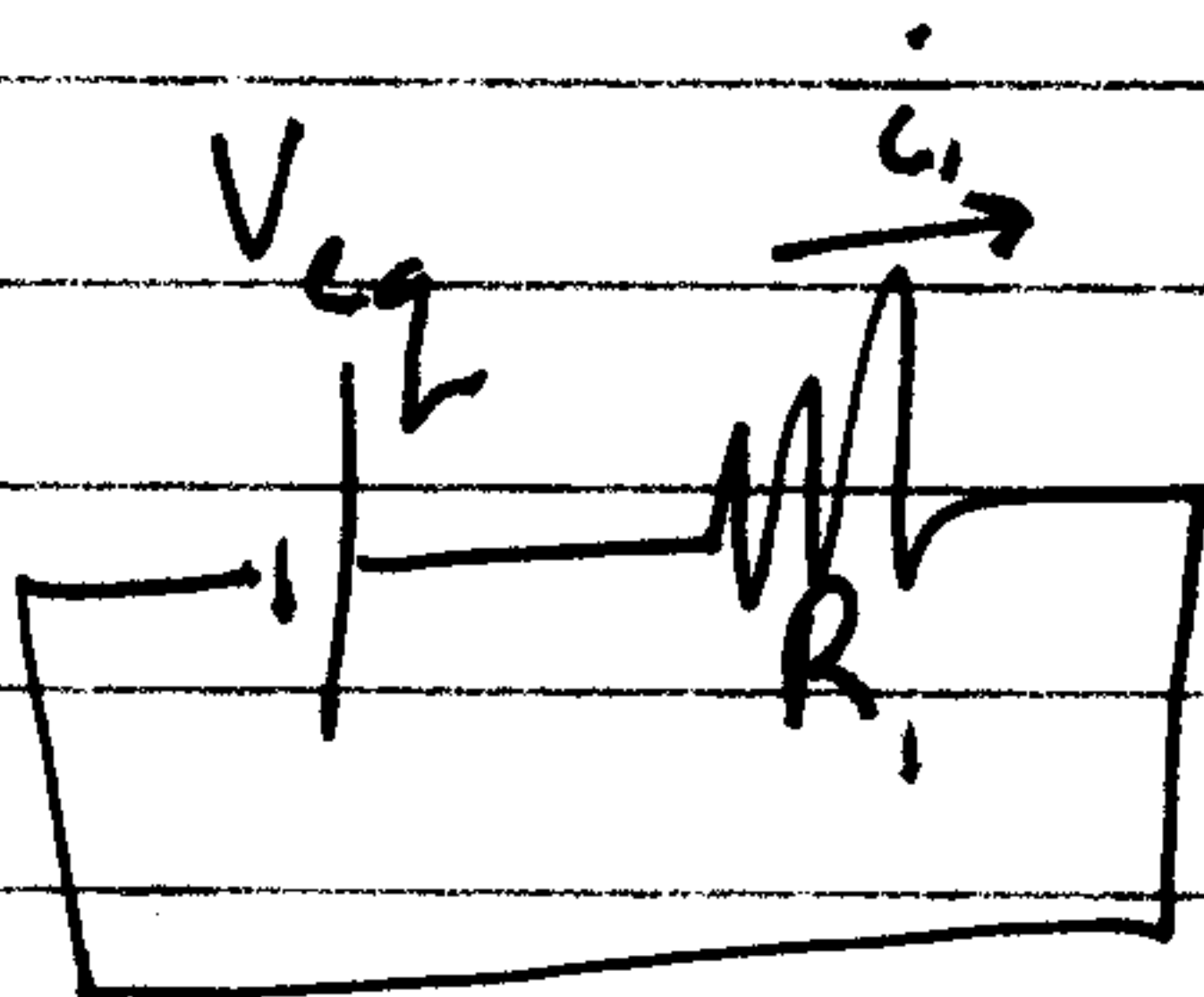4) The voltage across R_1 must be $= V_2$ (voltage of battery)

This means that we could have the eq. circuit



$$V_{eq} = V_1 + V_2 + V_3 = 15V$$



so $i_1 = \frac{15V}{100\Omega} = 0.15A$

$$= \frac{V}{R} = \frac{15V}{100\Omega} = 0.15A$$

b) since we know the voltage across R_2 is V_2

$$i_2 = \frac{V_2}{R_2} = \frac{5V}{50\Omega} = 0.1Amp$$

c)

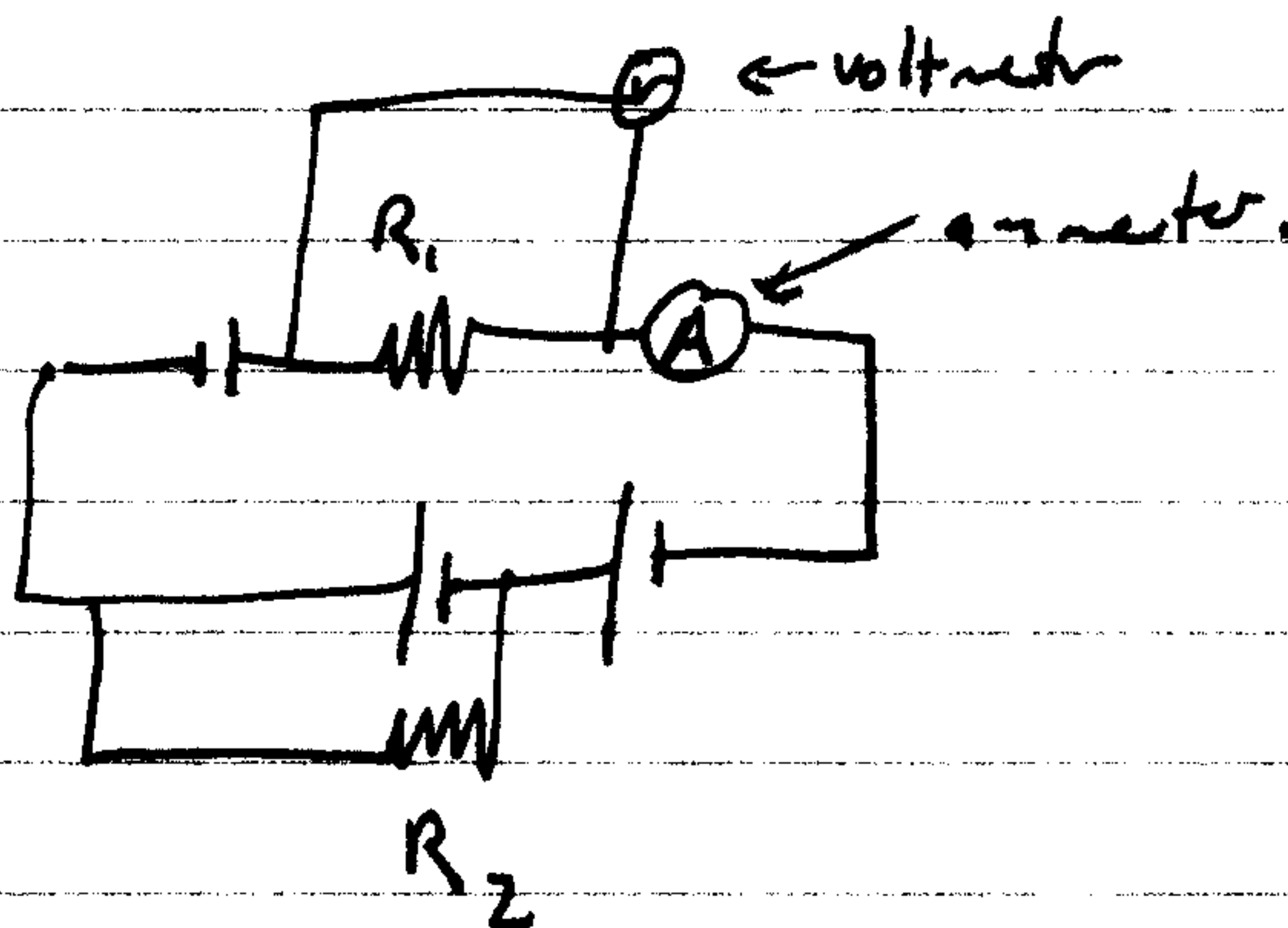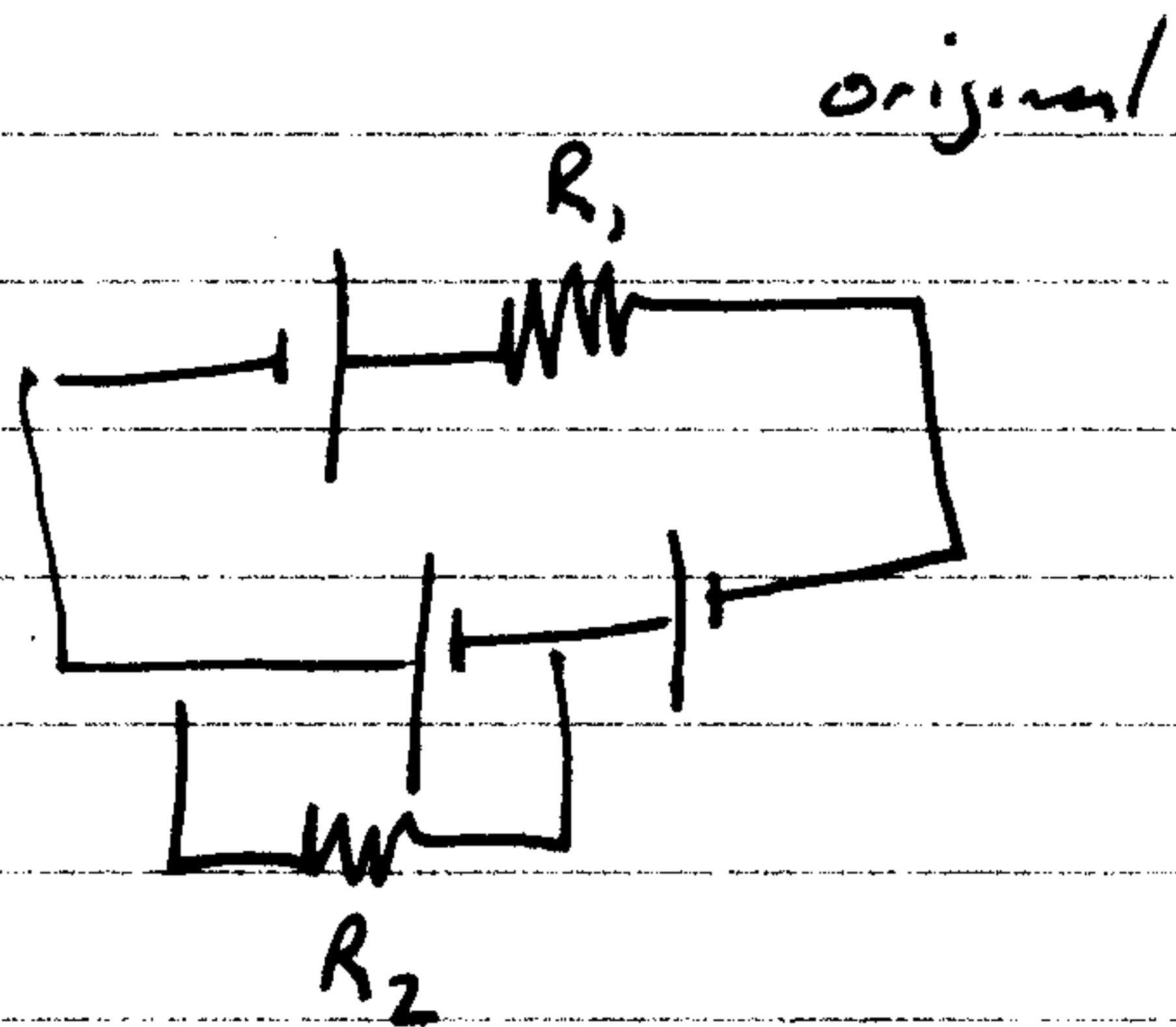


3 $Q = CV$

Now according to Gauss law

$$\frac{q_{enc}}{\epsilon_0} = \oint_{\text{closed surface}} \vec{E} \cdot d\vec{A}$$

$$= \oint_{\text{closed surface}} \|\vec{E}\| \|d\vec{A}\|$$

$$= \|\vec{E}\| 4\pi r^2$$

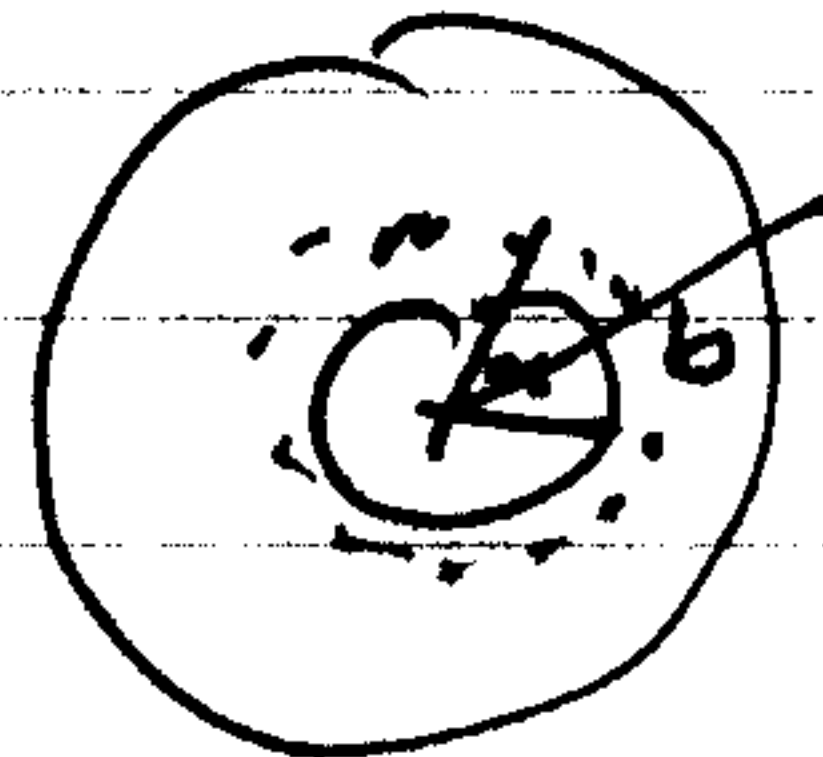


$$\|\vec{E}\| = \frac{q_{enc}}{4\pi\epsilon_0 r^2} = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$\Delta V = - \int_a^b \vec{E} \cdot d\vec{r} = - \int_a^b \frac{Q}{4\pi\epsilon_0 r^2} dr = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{r} \right]_a^b = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{b} - \frac{1}{a} \right)$$

$$\text{So } Q = \frac{4\pi\epsilon_0 \Delta V}{\frac{1}{b} - \frac{1}{a}}$$

$$= \left[\frac{4\pi\epsilon_0 ab}{a-b} \right] \Delta V$$

$$C = \frac{4\pi\epsilon_0 ab}{a-b}$$

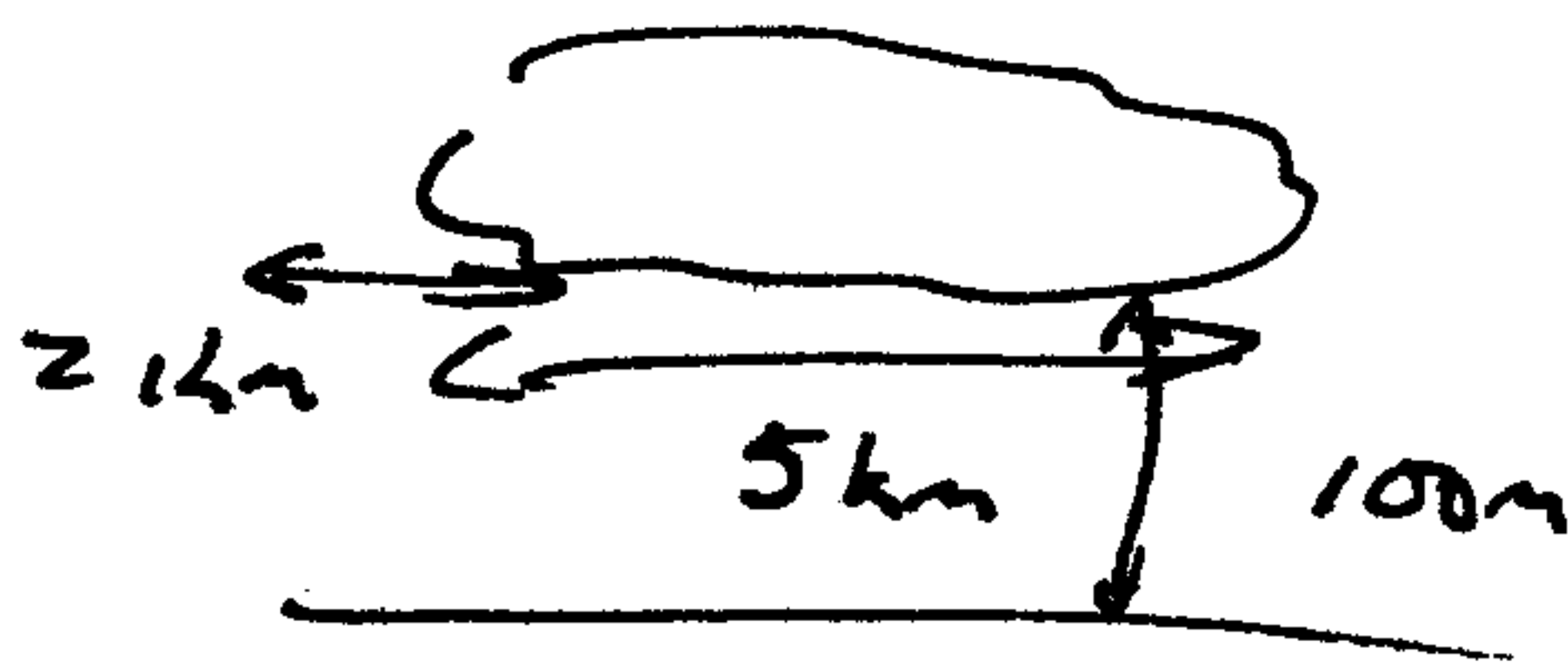


6 for parallel plate capacitors

$$\begin{aligned}
 \text{a)} \quad C &= \frac{\epsilon_0 A}{d} = \epsilon_0 \frac{5 \times 10^3 \text{ m} \times 2 \times 10^3 \text{ m}}{10^2 \text{ m}} \\
 &= 8.85 \times 10^{-12} \times 10^5 \\
 &= 8.85 \times 10^{-7} \text{ F} \\
 &= .885 \mu\text{F}
 \end{aligned}$$

$$\begin{aligned}
 \text{b)} \quad \Delta V &= 3 \times 10^8 \text{ V so} \\
 Q &= 8.85 \times 10^{-7} \text{ F} \times 3 \times 10^8 \text{ V} \\
 &= 266 \text{ C}
 \end{aligned}$$

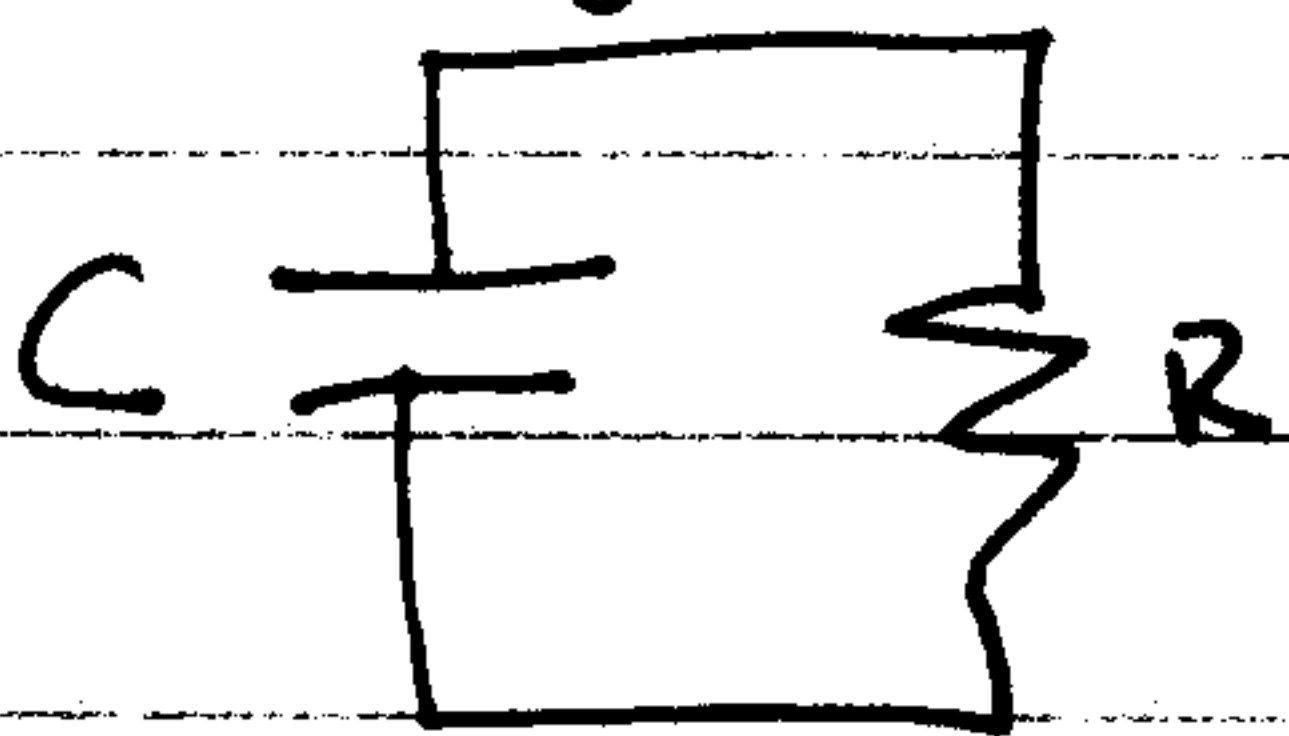c) through a resistor we have $V = iR$ where $V =$ voltage drop



$$Q = CV$$

The voltage across the capacitor will be

$$-iR \text{ so that}$$

$$Q = -iRC$$

$$-\frac{1}{RC} Q = \frac{dQ}{dt}$$

$$\frac{dQ}{dt} = -\frac{Q}{\tau} \quad \ln Q + Q_0 = -\frac{t}{\tau}$$

$$\begin{aligned}
 Q/Q_0 &= e^{-t/\tau} \\
 Q &= Q_0 e^{-t/\tau} \\
 &= 266 \text{ C} e^{-t/885 \text{ ns}}
 \end{aligned}$$

$$\begin{aligned}
 \text{d)} \quad u &= \frac{1}{2} CV^2 \\
 \Rightarrow \frac{u}{u_0} &= \frac{1}{2} CV^2 / \frac{1}{2} CV_0^2
 \end{aligned}$$

$$\begin{aligned}
 \frac{1}{2} &= \frac{V^2}{V_0^2} \\
 V &= V_0 / \sqrt{2}
 \end{aligned}$$

$$\text{or } Q = Q_0 / \sqrt{2}$$

$$e^{-t/\tau} = \frac{1}{\sqrt{2}}$$

$$t = \tau \ln \sqrt{2} = 30.7 \text{ ns}$$