

Power Electronics Chapter 7 and 8 HW

1. Use LT spice to build a buck-boost converter, use the schematic in Figure 7-18


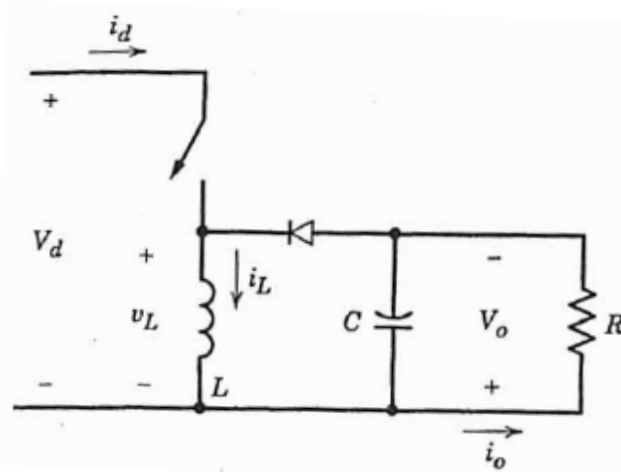


Figure 7-18 Buck–boost converter.

with the following device values:

- a) $C=50\mu\text{F}$
- b) $R=10\Omega$
- c) $L=100\mu\text{H}$
- d) $V_d=15\text{V}$
- e) switch=TIP32 pnp power transistor, operate the switch with a $5V_{pp}$ 25kHz square wave with a 50% duty cycle .
 - Is the converter in continuous or discontinuous mode? Justify your answer.
 - Calculate (by hand) the output voltage for this circuit.
 - Measure the average output voltage for this circuit and calculate the percent difference between the measured and predicted values.
 - Estimate the voltage ripple from your simulation.

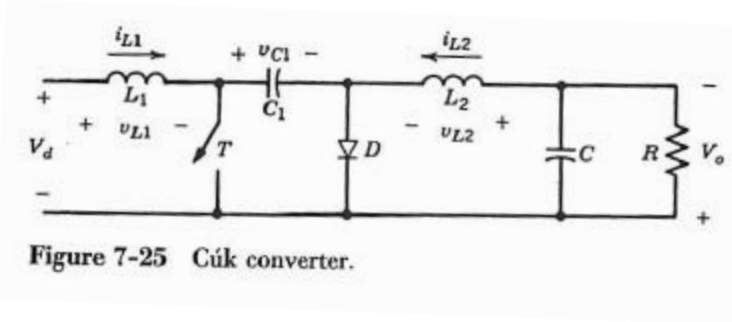2. Use LT spice to build a Cúk converter, use the schematic in Figure 7-25



with the following device values:

- $L_1=L_2=100\mu\text{H}$
 - $C_1=5\mu\text{F}$
 - $C=50\mu\text{F}$
 - $R=10\Omega$
 - $V_d=15\text{V}$
 - switch=TIP31 npn power transistor, operate the switch with a $5V_{pp}$ 25kHz square wave with a 50% duty cycle.
 - Is the converter in continuous or discontinuous mode? Justify your answer.
 - Calculate (by hand) the output voltage for this circuit.
 - Measure the average output voltage for this circuit and calculate the percent difference between the measured and predicted values.
 - Estimate the voltage ripple from your simulation.
3. The diode in a buck converter has a different purpose than a diode in a full bridge converter. Explain what the diode in each circuit is for.

4. For the circuit in Figure 7.27

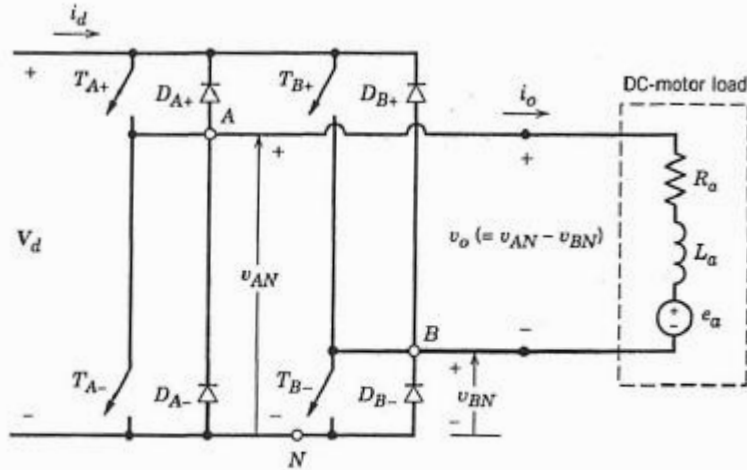


Figure 7-27 Full-bridge dc-dc converter.

explain how to

- operate the switches to make current flow through the motor in the direction shown by the arrow i_o with a voltage V_d across the motor,
 - operate the switches to make current flow through the motor against the direction shown by the arrow i_o with a voltage V_d across the motor,
 - operate the switches to make current flow through the motor in the direction shown by the arrow i_o with a voltage $V_d/3$ across the motor.
 - Show that you were correct in part c by building an LTspice simulation using:
 - TIP transistors
 - $R_a=2\Omega$
 - $L_a=10\text{mH}$
 - $e_a=10\text{V}$
 - $V_d=15\text{V}$
- What is the difference between a full bridge DC->DC converter and an inverter?
 - Consider a load driven by an inverter powered by a battery. If the load creates reactive power what happens to it (e.g., where does the current flow)?
 - In class we stitched together two buck converters to make an inverter. We then looked at an LTspice implementation of that circuit (attached) but didn't put in the free-wheel diodes. Explain where the free-wheel mechanism should go and what circuit element(s) you would use to make the free-wheel.