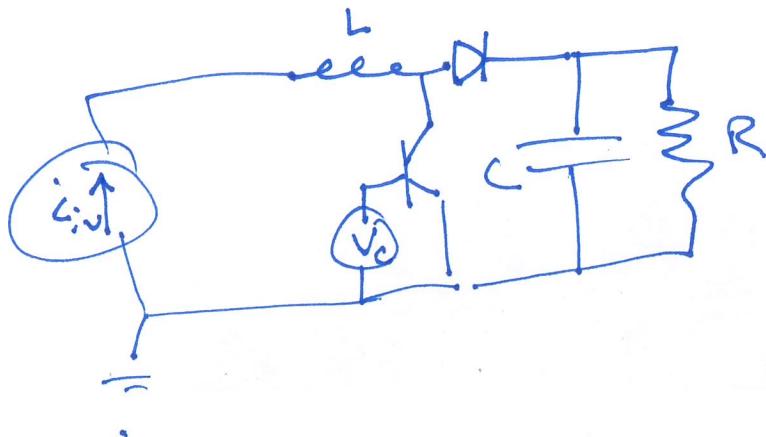


Step-up (Boost Converter)

this makes more sense w/ a current source than a voltage source




w/ a current source the current flowing through the inductor is steady

$i_L = i_{in}$ it is where the current goes after leaving the inductor that shifts below to the transistor.

Since


$$\frac{di_L}{dt} = \frac{1}{L} V_L \text{ we have } V_L = 0.$$

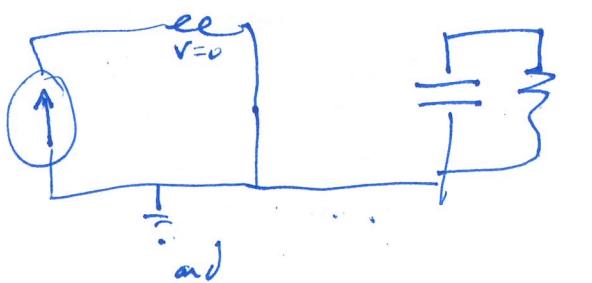so w/ V_C high the ~~transistor~~ ^{transistor} conducts and our circuit becomes



and
 $V_{in} = 0$ for on-state

w/ V_C low

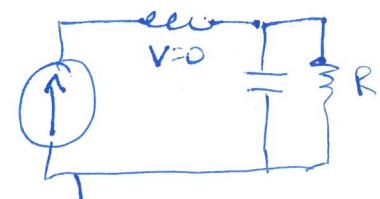

$$V_{out} = V_L + V_{in} \\ = V_{in} \\ \text{for } -t_{on} < t < T$$

w/ C large $\langle V_{out} \rangle$ is steady

$$\langle V_{in} \rangle = \frac{1}{T} \int_0^T V_{in} dt = \frac{1}{T} \int_0^{t_{on}} V_{in} dt + \frac{1}{T} \int_{t_{on}}^T V_{in} dt = 0 + \frac{1}{T} V_{in}(T-t_{on})$$

$$\langle V_{in} \rangle = V_{out} \left(1 - \frac{t_{on}}{T}\right) = V_{out} (1-D)$$

and

$$V_{out} = \frac{\langle V_{in} \rangle}{1-D}$$

Considering the current recall that $\langle i_{cap} \rangle = 0$ in steady state

$$\text{so } \langle i_{load} \rangle = \langle i_{diode} \rangle$$

$$\begin{aligned} \langle i_{load} \rangle &= \frac{1}{T} \int_0^T i_{diode} dt \\ &= \frac{1}{T} \int_0^{t_{on}} i_{diode} dt + \frac{1}{T} \int_{t_{on}}^T i_{diode} dt \\ &\quad \uparrow \qquad \qquad \downarrow \\ &\quad D, \text{ diode is reverse biased} \\ &= \frac{1}{T} i_{in} (T - t_{on}) = i_{in} (1-D) \end{aligned}$$

and

$$\begin{aligned} P_{out} = \langle V_{out} \rangle \langle i_{load} \rangle &= \frac{\langle V_{in} \rangle}{1-D} i_{in} (1-D) \\ &= \langle V_{in} \rangle i_{in} \end{aligned}$$

Notice that the transistor is again shutting off the power from the current source, a voltage source yields the same relationship by shorting it.

BETWEEN $\langle V_{in} \rangle, \langle V_{out} \rangle, \langle i_{in} \rangle$ and $\langle i_{out} \rangle$

w/ much larger variation in $i_L(t)$

for a current source,

all values of D


yield a continuous current through i_L

for a voltage source

~~is continuous~~


i_L is only cont. for some values of D .

Buck-Boost Converter

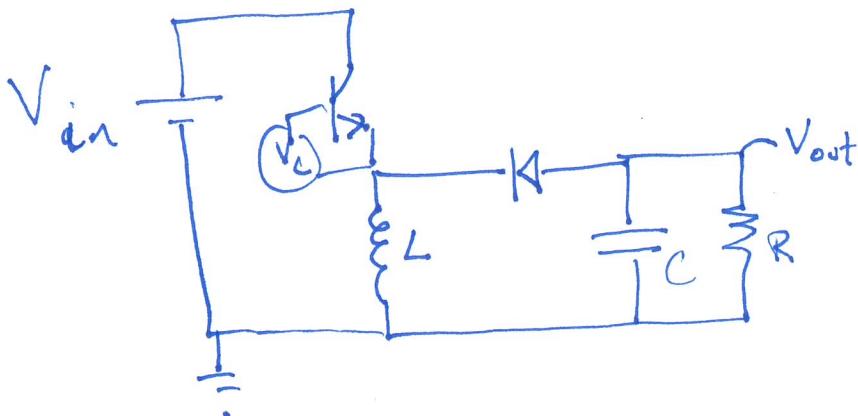


1st thing to note, current only leaves R/C combo going through a forward biased diode. This means that $V_{out} < 0$ while $V_{in} > 0$. The buck-boost circuit flips the sign of the output wrt input.

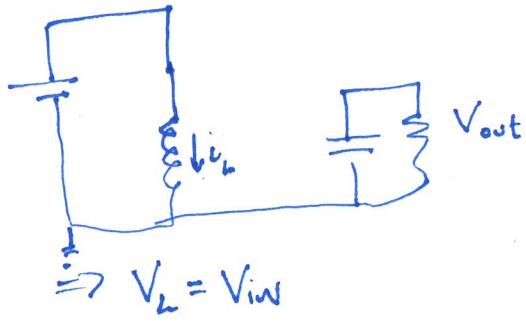when V_C is high
the circuit simplifies to



$$\Rightarrow V_L = V_{in}$$

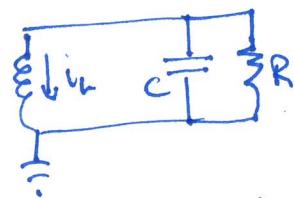when V_C is low
the circuit simplifies to



$$V_L = V_{out}$$

$$\begin{aligned} \langle V_L \rangle &= \frac{1}{T} \int_0^T V_L dt = \frac{1}{T} \int_0^{t_{on}} V_{in} dt + \frac{1}{T} \int_{t_{on}}^T V_{out} dt = 0 \\ &= \frac{1}{T} t_{on} V_{in} + \frac{1}{T} (T - t_{on}) V_{out} = 0 \end{aligned}$$

$$DV_{in} = -(1-D)V_{out}$$

$$V_{out} = \frac{-D}{1-D} V_{in}$$

You can think of the inductor as being like a flywheel.
inductor can get overloaded if R is too low