

# EXPERIMENT 8: LRC CIRCUITS

---

## Equipment List

- S<sub>1</sub> BK Precision 4011 or 4011A 5 MHz Function Generator
- OS BK 2120B Dual Channel Oscilloscope
- V<sub>1</sub> BK 388B Multimeter
- L<sub>1</sub> Leeds & Northrup #1532 100 mH Inductor
- R<sub>1</sub> Leeds & Northrup #4754 Decade Resistor
- C<sub>3</sub> Cornell-Dubilier #CDA2 Decade Capacitor
- C<sub>2</sub> Cornell-Dubilier #CDB3 Decade Capacitor

## Introduction

Consider the LRC circuit drawn to the right. According to Kirchoff's Law, at any time after the switch is closed we must find

$$V = V_R + V_C + V_L$$

$$V = iR_t + \frac{Q}{C} + L \frac{di}{dt}$$

where the total resistance in the circuit is the sum of the external resistance and the internal resistance of the inductance; i.e.  $R_t = R + R_L$ . Taking account of the relation  $dq/dt = i$ , after the switch is closed, the derivative of this equation is

$$\frac{dV}{dt} = R_t \frac{di}{dt} + \frac{1}{C} i + L \frac{d^2i}{dt^2} \quad (2)$$

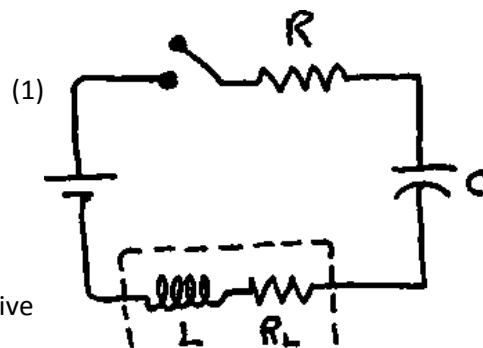


Figure 1: LRC Circuit

A solution to this second order differential equation is known to be damped harmonic and, for the initial conditions  $q = i = 0$ , given by

$$i = \frac{V}{L\sqrt{\delta}} e^{-\frac{R_t}{2L}t} \sin[(\sqrt{\delta})t] \quad (3)$$

This equation contains an exponential damping term times a sine wave term where the frequency of the sine wave is

$$\omega = \sqrt{\delta} \quad \delta = \frac{1}{LC} - \frac{R_t^2}{4L^2} \quad (4)$$

## Experiment 8, RLC Resonant Circuits

This solution has three regions of interest:

1. **underdamped** ( $\zeta < 1$ ) - the solution is damped oscillations
2. **overdamped** ( $\zeta > 1$ ) - the argument of the sine function is complex; thus, the sine function becomes a real exponential
3. **critically damped** ( $\zeta = 1$ ) - the current returns to zero in the shortest possible time.

It should be recognized that in any circuit which undergoes an abrupt change in voltage these effects will be present. Case one is the most frequent and is called ringing.

In an alternating current LRC circuit the change in voltage with time in equation 2 is no longer zero, and whatever transient effects due to the turning on of the AC generator will quickly disappear. For a sine wave input, the solution to equation 2 is also a sine wave. For the series circuit, the current is the same through all components. As we observed last week, the voltage across the capacitor lags the current by  $90^\circ$ . Thus,  $V_L$  and  $V_C$  are  $180^\circ$  out of phase with one another in the series circuit. If we choose the phase of the current to be zero, the current can be written as

$$i_s = I \sin(\omega t) \quad (5)$$

Then the source voltage is

$$v_s = V \sin(\omega t + \phi) \quad (6)$$

where the source voltage leads the current by the phase angle

$$\phi = \tan^{-1} \left( \frac{\omega L - 1/\omega C}{R} \right) \quad (7)$$

The phase angle can be illustrated by the vector representation in Figure 3. In this example the inductive reactance  $X_L = \omega L$  is greater than the capacitive reactance  $X_C = 1/\omega C$ , thus, the phase angle is positive and the source voltage leads the source current. For a constant amplitude source

$$I = \frac{V}{Z} \quad (8)$$

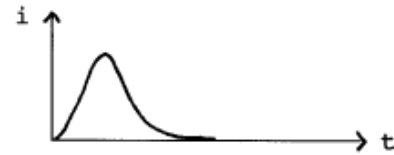
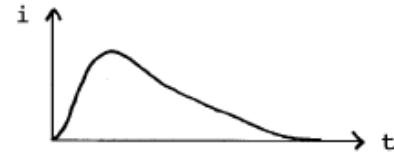
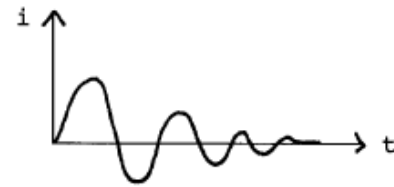


Figure 2: Underdamped, Overdamped, and Critically Damped LRC Circuit Response

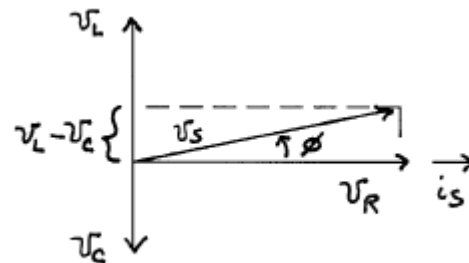


Figure 3 Phase Relationships

## Experiment 8, RLC Resonant Circuits

where the impedance  $Z$  is given by

$$Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2} \quad (9)$$

The important difference between the LRC circuit and that of either the RC or RL circuits is that the current does not asymptotically increase or decrease but has a maximum. Note the behavior of the impedance

$$Z \rightarrow \begin{cases} \infty & \text{as } \omega \rightarrow 0 \\ \infty & \text{as } \omega \rightarrow \infty \end{cases} \quad (10)$$

Note that the current goes to zero when the impedance becomes infinite. Thus, the current is zero for zero frequency, peaks for some finite frequency, and then drops to zero for large frequencies. The current reaches a maximum when the impedance is a minimum, or equivalently, for that frequency where the capacitive and inductive reactances are equal; i.e., from equation 9

$$\omega_o L - \frac{1}{\omega_o C} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{LC}} \quad (11)$$

This type of circuit is a selective filter and is the basis for tuning in radios and TVs, etc. A measure of how sharp the resonance peak is, or the fineness of tuning, is called the Q factor of the circuit. The Q value is defined as the inverse of the fractional bandwidth.

$$\frac{1}{Q} = \frac{\Delta\omega}{\omega_o} = \frac{\Delta f}{f_o} \quad (12)$$

In an LRC series circuit the Q value can be calculated for R not too large as

$$Q = \frac{\omega_o L}{R} \quad (13)$$

## Part I: RC rehash

Re-build the low pass filter from lab 4 shown in Fig. 4

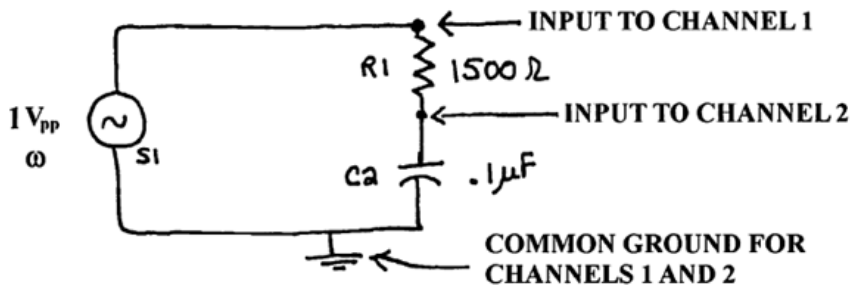


Figure 4: Low-pass RC filter

Sweep from low frequencies to high frequencies and observe how the output (Channel 2) depends on frequency. This is typical for a first order system. Estimate the cut-off frequency from what you see on the oscilloscope.

## PartII: Ringing

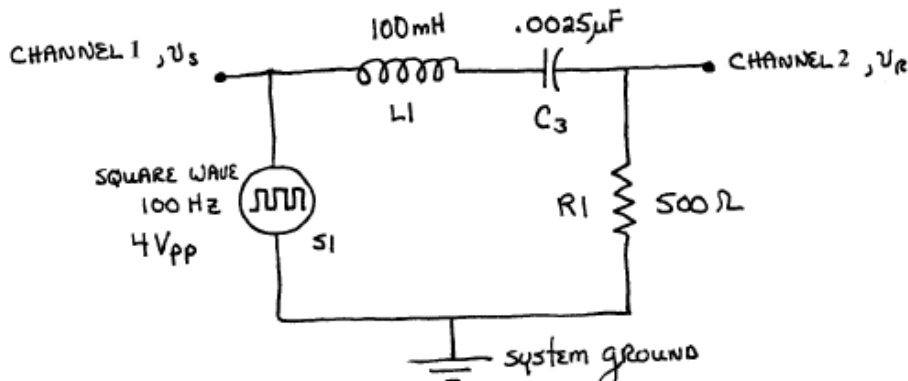


Figure 5: Laboratory Setup for Ringing

- Measure the resistance of the inductor  $L_1$  with your multimeter.
- Construct the circuit shown above. This should produce an underdamped circuit.
- Using Eqs. 4, calculate  $\delta$  and then from Eq. 3 the frequency of oscillation,  $f(\delta)$ .
- Measure the actual frequency from Channel 2.
- Vary  $R$  and  $C$  around the given values.

Question 1: What are the most obvious effects of changing  $R$  and  $C$ ? Answer in terms of Eqs. 3 and 4.

- For  $L = 100 \text{ mH}$  and  $R = 500 \Omega$ , calculate the value of  $C$  that produces critical damping.
- Adjust  $C$  for critical damping on the oscilloscope.

## Experiment 8, RLC Resonant Circuits

Question 2: Can you guess why there is a discrepancy between the actual C and the calculated C to produce critical damping?

### Part III: Resonance

- a. Set up the following circuit to determine the resonance frequency of the circuit experimentally.

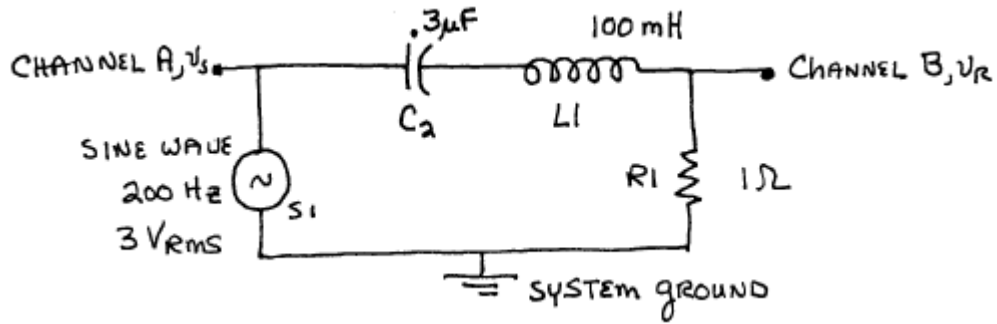


Figure 6 Series Resonance Circuit

*Note:* The  $1.0\Omega$  resistor is a current transducer, turning current into voltage by Ohms Law.

- Look for a resonance around 900 Hz. Remember to maintain the source voltage constant. The resonance is reached when  $V_R$  is a maximum. When you find resonance frequency, make many measurements around the resonance.
- Measure  $I_R$  as a function of frequency about the resonance.
- Plot  $I_R^2$  versus frequency on the computer. This curve is proportional to power.
- Determine the resonance frequency  $f_0$  and the bandwidth  $\Delta f$  from your plot.

## Part IV: The Transformer

In a transformer made up of two coils of wire, one inside the other, the voltage developed across the loops is not resistive in the sense of an IR drop, but is given by Faraday's law as

$$V_1 = -N_1 \frac{d\Phi_B}{dt} \quad (14)$$

where  $\Phi$  is the magnetic flux through each loop. If we assume that all of the magnetic field lines from loop 1 go through loop 2, as shown, then the change in flux/loop in loop two is just the change in flux/loop in loop one; thus, there is an EMF developed in the second loop given by

$$V_2 = -N_2 \frac{d\Phi_B}{dt} \quad (15)$$

where the difference in EMF's is due to the different number of turns in the two loops. In both loops the rate of change of the magnetic flux with time is the same. We can use this fact to show that the EMF's of the two coils can be related by

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad (16)$$

which says that the ratio of voltages between loops one and two goes as the ratio of the number of turns (i.e. the turns ratio).

- a. Connect the input leads of the oscilloscope to the inner coil (secondary) of the transformer. These leads are at the top of the transformer. Make sure the iron rod is in place inside the secondary. Connect the even numbered table terminals to the outer coil (primary) of the transformer. These leads are at the base of the transformer.
- b. Measure and record the peak-to-peak voltage of the secondary.
- c. Measure the peak-to-peak voltage of the primary and use this to determine the turns ratio from equation 16.
- d. Slowly pull the secondary out from the primary holding the rod to the secondary. Since the magnetic flux of the primary no longer goes completely through the secondary you should observe a decrease in the secondary voltage. Replace the secondary coil.
- e. Slowly pull the iron rod out from the secondary coil then replace it. The iron rod plays a central role in confining the magnetic field lines inside the secondary. Its removal also acts to decrease the secondary voltage.

Question 3: What happened when you pulled the secondary coil out? What happened when you pulled the iron rod out? Why does this make sense?

Experiment 8, RLC Resonant Circuits

Name: \_\_\_\_\_

**Part I:**

Cut-off frequency

**Part II:**

$R_L =$

$\delta =$

$f(\delta) =$

$f(\text{measured}) =$

Question 1:

$C(\text{theory}) =$

$C(\text{measured}) =$

Question 2:

**Part III: (staple graph)**

$L =$

$R_L =$

f(Hz)	i	$i^2$
200		
5000		
$f_0 =$	$\omega_0 =$	

Experiment 8, RLC Resonant Circuits

**Part IV:**

Peak-to-Peak Secondary Voltage =

Peak-to-Peak Primary Voltage =

Turns Ratio =