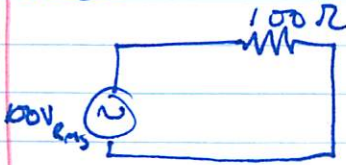



Electronics HW #3

2.35



$$\langle P \rangle = i_{RMS} V_{RMS} = \frac{V_{RMS}^2}{R} = \frac{(100V)^2}{100\Omega} = 100W$$

2.36

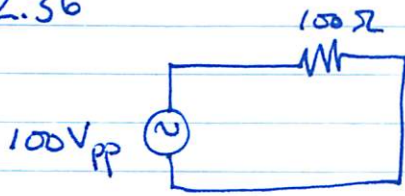


$$V_{\text{amplitude}} = \frac{V_{PP}}{2} = 50V$$

$$V_{RMS} = \frac{\text{Amplitude}}{\sqrt{2}} = \frac{50V}{\sqrt{2}}$$

$$\langle P \rangle = \frac{V_{RMS}^2}{R} = \left(\frac{50V}{\sqrt{2}}\right)^2 \frac{1}{100\Omega} = 12.5W$$

2.39

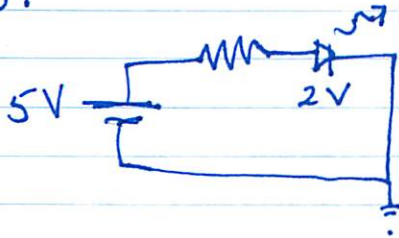

By Kirchhoff's loop rule

$$5V - iR - 2V = 0$$

$$R = \frac{3V}{i}$$

The desired current is at least $i = 10 \times 10^{-3} A$
and at most $i = 100 \times 10^{-3} A$

$$\text{so } R = \frac{3V}{10^{-2} A} = 300\Omega$$

$$\text{and } R = \frac{3V}{10^{-1} A} = 30\Omega$$

$$30\Omega < R < 300\Omega$$


The power dissipated will depend on R

$$P = \frac{V^2}{R} = \frac{9V^2}{30\Omega} \text{ to } \frac{9V^2}{300\Omega} = 0.3W \text{ to } 0.03W$$


so a 1/2W resistor w/

$$30\Omega < R < 300\Omega$$

would work.

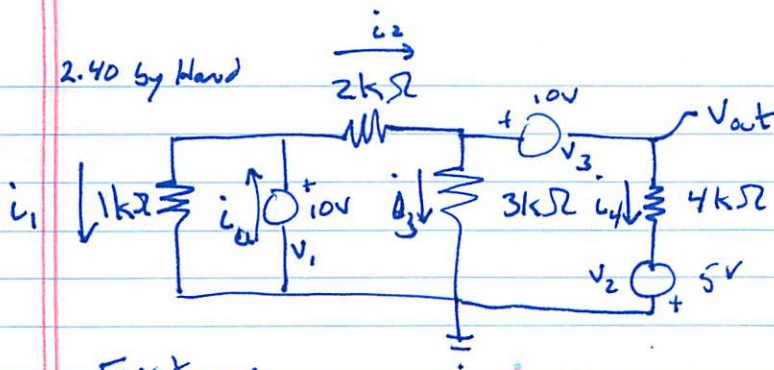

First we ~~then~~ assign current directions and then write loop and node equations

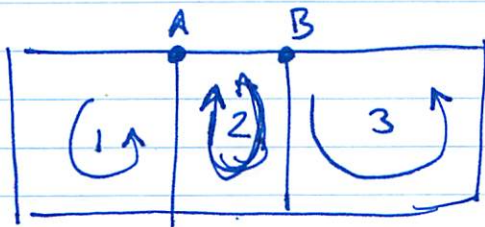

loop 1

$$10V - i_1 1k\Omega = 0$$

loop 2

$$10V - 2k\Omega i_2 - 3k\Omega i_3 = 0$$

loop 3

$$10V - 3k\Omega i_3 - 5V + 4k\Omega i_4 = 0$$

Node A

$$i_a = i_1 + i_2$$

Node B

$$i_2 = i_3 + i_4$$

from loop 1 $i_1 = 10mA$

Combining loop 2 and Node B

$$10V - 2k\Omega (i_3 + i_4) - 3k\Omega i_3 = 0$$

$$10V - 5k\Omega i_3 - 2k\Omega i_4 = 0$$

simplify loop 3

$$5V - 3k\Omega i_3 + 4k\Omega i_4 = 0$$

$$25V - 13k\Omega i_3 + 0 = 0$$

$$\text{or } i_3 = \frac{25}{13} mA = 1.92 mA$$

and from loop 3 $5V - \frac{75}{13} V = -4k\Omega i_4 \Rightarrow i_4 = 0.19mA$ or $\frac{5}{26} mA$

Taking stock we want V_{out} , P_{V_1} , P_{V_2} , P_{V_3}

$$V_{out} = i_y R_y - 5V = 0.19 \text{ mA} \times 4 \text{ k}\Omega - 5V = -4.23V$$

To find Powers

$$P_{V_1} = i_a (V_1) = i_a 10V$$

$$P_{V_2} = i_y (+V_2) = 0.19 \text{ mA} (+5V) = +0.96 \text{ mW} \quad \leftarrow \text{adds power}$$

$$P_{V_3} = i_y (-V_3) = 0.19 \text{ mA} (-10V) = -1.9 \text{ mW} \quad \leftarrow \text{removes power}$$

all that remains is i_a which from nodes A & B is

$$i_a = i_1 + i_3 + i_y = 10 \text{ mA} + 1.92 \text{ mA} + 0.19 \text{ mA} = 12.12 \text{ mA}$$

so

$$P_{V_1} = 121.2 \text{ mW} \quad \leftarrow \text{adds power}$$

Comparing this w/ LTspice (see HW3b.pdf)

$$V_{out} = -4.23V$$

$$P_{V_1} = -121.15 \text{ mW}$$

$$P_{V_2} = -0.96 \text{ mW}$$

$$P_{V_3} = 1.92 \text{ mW}$$

Note that LTspice reports dissipated power so negative power \Rightarrow power added to circuit.

2.46 Power in
from wall
120V_{rms}

Power out
to lights
24V_{rms}

we need to step down the voltage

$$\begin{aligned} \text{in} &\rightarrow \frac{V_p}{V_s} = \frac{n_p}{n_s} \\ \text{out} &\rightarrow \end{aligned}$$

$$\frac{120 \text{ V}}{24 \text{ V}} = 5 = \frac{n_p}{n_s} \quad \text{we need 5x as many primary loops as secondary.}$$

2.47 Impedance matching delivers maximum power
so if $Z_{out} = 8\Omega$ we need $Z_{in} = 8\Omega = \text{impedance}$
of speaker to choose.

2.48 Separate wires can gap forming a loop i.e.
an inductor. This inductor can pick up high frequency
interference, it acts like an antenna.