

## Practice Exam #2 Sol<sup>n</sup>s


1) From the equation raising  $T$  has the same effect as lowering  $V_D$ . Increasing  $T$  will reduce the current that flows effectively raising the resistance of the diode.

2) a) find  $V_{out}$  w/  $V_s = +10V$  -

$V_{cap}$   
 $i_{cap}$   
 $i_{R3}$

which implies the diode will conduct and the cap will be charged w/ no current flowing so

the equivalent circuit is

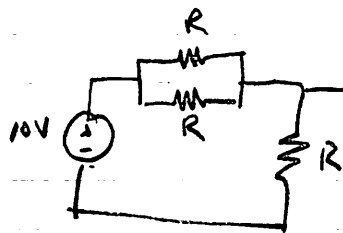


voltage divider

$$V_{out} = \frac{R}{R+R/2} \cdot 10V = \frac{20}{3}V = 6.7V$$

this is also  $V_{cap}$ ,  $i_{cap} = 0$

$$i_{R3} = \frac{V_{out}}{R} = \frac{1}{R} 6.7V$$

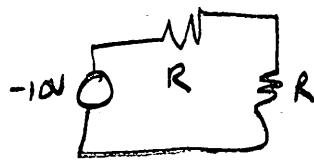b) here  $V_s = -10V$  and the diode will not conduct, cap will be full so





$$V_{out} = \frac{R}{2R} (-10V) = -5V = V_{cap}$$


$$i_{cap} = 0, \quad i_{R3} = \frac{V_{out}}{R} = \frac{1}{R} 5V$$

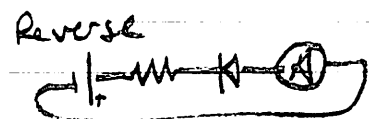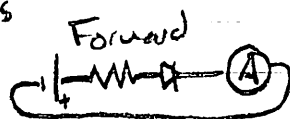3) In the forward biased state there is no difference, it is in the reverse-biased state that things change. Regular diodes never conduct (in principle) or only do so catastrophically (in practice). Zener diodes break down non destructively and pass current w/ a voltage drop  $V_Z$  across the device.

Experimentally, both will conduct forward biased @  $\sim 0.7V$  reverse biased the zener will conduct at a moderately high reverse bias



4] 3.18 a)

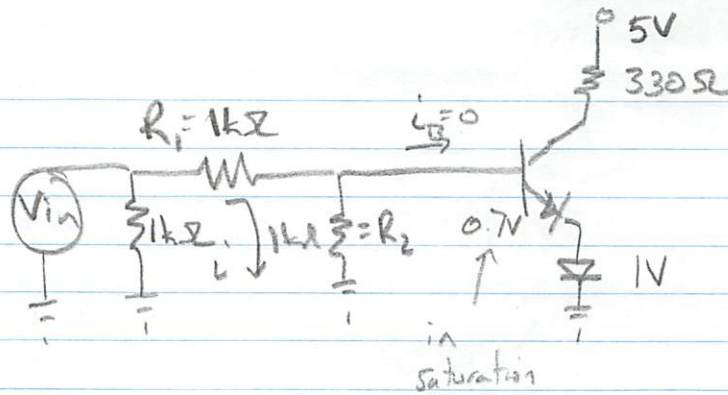


in on state

$$V_b = 1.7V = i \cdot 1k\Omega \Rightarrow i = 1.7mA$$

$$V_{in} = i(2k\Omega) = 3.4V \quad \left( \begin{array}{l} \text{there are 2} \\ \text{resistor in} \\ \text{series w/} \\ \text{current } i \\ \text{between } V_{in} \text{ \& } \text{ground} \end{array} \right)$$

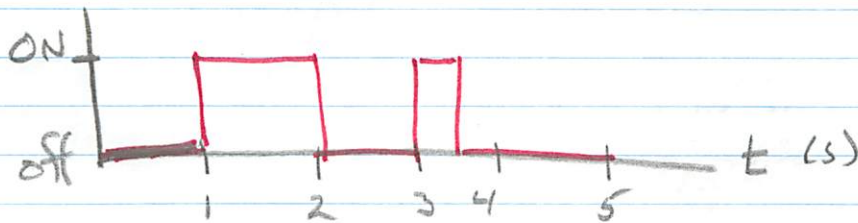so, if  $V_{in} < 3.4V$  LED is off, if  $V_{in} > 3.4V$  LED is on,



b) Now w/  $\beta \neq \infty$ ,  $\beta = 100$

$$\beta i_b = i_c$$

And in saturation the voltage across the collector resistor is

$$V_{R_c} = 5V - 1V - 0.2V$$

$$= 3.8V = i_c R$$

$$i_c = \frac{3.8V}{330\Omega} = 11.5mA$$

$$\text{so } i_b = i_c / \beta = 0.115mA$$

$$\begin{aligned} \text{Now } V_{in} &= (i + i_b)R + iR = (2i + i_b)R \\ \text{to turn on in saturation} &= (2 \times 1.7mA + 0.115mA) 1k\Omega \\ &= 3.515mA \times 1k\Omega \\ &= 3.515V \text{ vs } 3.4V, \end{aligned}$$

5) The transistor is an n-channel MOSFET transistor. The diode is there as a fly back diode to protect the transistor from damage from arcing when the transistor is shut off ( $v = L di/dt$ ).

6) a) No, it is not even periodic

b) yes and  $\omega_0 = 1.8 \text{ rad/s}$

c) No, the frequencies of the terms are not integer multiples of a fundamental frequency  $\omega_0$ .

d) yes,  $\omega_0 = 1.8 \text{ rad/s}$ .

7) There are 2 bands w/  $\omega_{L1} = 1.5 \text{ rad/s}$   $\omega_{H1} = 2.9 \text{ rad/s}$   
 $\omega_{L2} = 6.1 \text{ rad/s}$   $\omega_{H2} = 10.2 \text{ rad/s}$

this assumes response is  $V_{out}/V_{in}$

8) a) No - no oscillation  
 b) No - no oscillation  
 c) possible, if system is underdamped otherwise it is just a decay like for 1st order.

