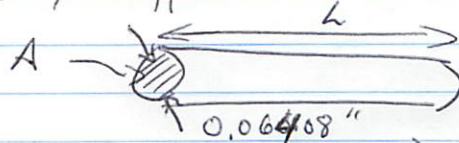


# Electronics Home Work Sol<sup>n</sup>s Problem set 1

2.1, 2.3, 2.10, 2.16, 2.17, 2.19, 2.21

2.1 The resistance of a piece of copper is

$$R = \frac{\rho L}{A}$$



$\rho = 1.7 \times 10^{-8} \Omega \cdot m$  (according to the text)  
 Note that this value is only correct if  $T \approx 20^\circ C$ ,  
 @  $250^\circ C$  the resistivity is about twice as much  
 (Source: Engineering toolbox.com)

$$R = \frac{1.7 \times 10^{-8} \Omega \cdot m \cdot 10^3 m}{\frac{\pi}{4} (0.06408 \text{ inch} \times 2.54 \times 10^{-2} \frac{m}{\text{inch}})^2}$$

$$= 8.2 \Omega \quad (@ 20^\circ C)$$

which is similar to the NEC value @  $75^\circ C$   
 of  $10.1 \Omega$  for solid wire  
 and  $10.3 \Omega$  for stranded wire

2.3

$$R_1 = 10 \times 10^2 \pm 5\% = 1 \times 10^3 \pm 50 \Omega$$

$$R_2 = 25 \times 10^1 \pm 5\% = 250 \pm 1.25 \Omega$$

(Chapter 9, table 8  
 NEC 2014)

$$\frac{1}{R_{eq}} = \frac{1}{250 \Omega} + \frac{1}{1000 \Omega} = \frac{5}{1000 \Omega} = \frac{1}{200 \Omega}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\delta R_{eq} = \sqrt{\left(\frac{\partial R_{eq}}{\partial R_1} \delta R_1\right)^2 + \left(\frac{\partial R_{eq}}{\partial R_2} \delta R_2\right)^2}$$

$$\frac{\partial R_{eq}}{\partial R_1} = -\frac{1}{R_1^2} \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^2$$

$$= \sqrt{\frac{4}{R_1^4} \delta R_1^2 + \frac{R_{eq}^4}{R_2^4} \delta R_2^2}$$

$$= \left(\frac{R_{eq}}{R_1}\right)^2$$

$$\frac{\delta R_{eq}}{R_{eq}} = R_{eq} \sqrt{\frac{1}{R_1^2} \left(\frac{\delta R_1}{R_1}\right)^2 + \frac{1}{R_2^2} \left(\frac{\delta R_2}{R_2}\right)^2}$$

$$= \frac{R_{eq}}{R_1} \delta R_1 \sqrt{\frac{1}{R_1^2} + \frac{R_1^2}{R_2^2}} = 5\% \times \frac{200 \Omega}{1000 \Omega} \sqrt{1 + 4^2}$$

$$= 5\% \times \frac{\sqrt{17}}{5} = 4\%$$

2.3 cont. to find the tolerance we need to propagate the uncertainty in  $R_1$ ,  $\delta R_1$ , and  $R_2$ ,  $\delta R_2$  into  $\delta R_{eq}$ .

by standard error propagation

$$\delta R_{eq} = \sqrt{\left(\frac{\partial R_{eq}}{\partial R_1}\right)^2 \delta R_1^2 + \left(\frac{\partial R_{eq}}{\partial R_2}\right)^2 \delta R_2^2}$$

$$\frac{\partial R_{eq}}{\partial R_1} = \frac{\partial \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}}{\partial R_1} = \frac{1/R_1^2}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)^2} = \left(\frac{R_{eq}}{R_1}\right)^2$$

so

$$\delta R_{eq} = \sqrt{\left(\frac{R_{eq}}{R_1}\right)^4 \delta R_1^2 + \left(\frac{R_{eq}}{R_2}\right)^4 \delta R_2^2}$$

or


$$\frac{\delta R_{eq}}{R_{eq}} = \frac{R_{eq}}{R_1} \sqrt{\frac{\delta R_1^2}{R_1^2} + \left(\frac{R_1}{R_2}\right)^2 \left(\frac{\delta R_2}{R_2}\right)^2}$$

$$= \frac{200}{1000} \sqrt{(0.05)^2 + \left(\frac{1000}{250}\right)^2 (0.05)^2}$$

$$= \frac{1}{5} \cdot 0.05 \sqrt{1+16} = 0.04 \approx 5\%$$


so

Red black brown gold is equivalent.

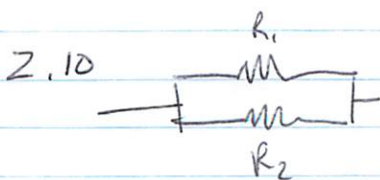

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{or} \quad \frac{R_2}{1 + R_2/R_1}$$

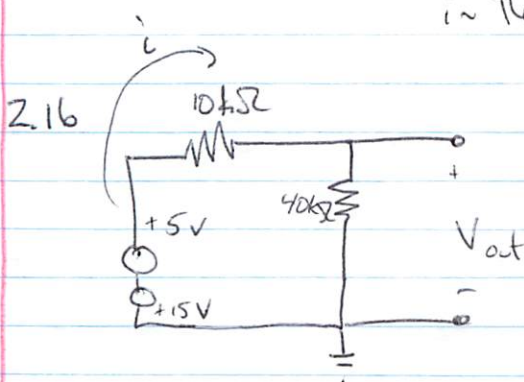in the limit  $R_2/R_1 \rightarrow 0$   $R_{eq} \Rightarrow \frac{R_2}{1+0} = R_2$




using kirchhoff's voltage law starting @ ground we have

$$-15V + 5V - i \cdot 10k\Omega - i \cdot 40k\Omega = 0$$

$$50k\Omega i = -10V$$

$$i = -\frac{1}{5} \text{ mA}$$

$$V_{out} = i \cdot 40k\Omega = -8V$$

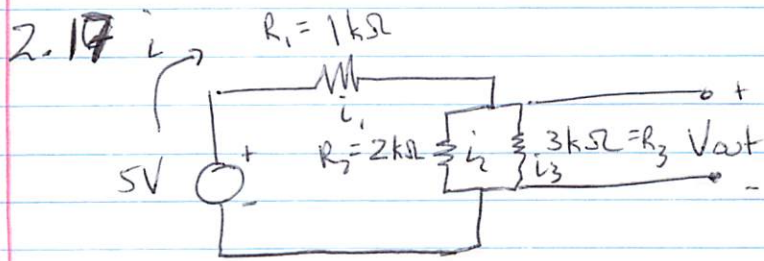

first the equivalent resistance for  $R_2$  &  $R_3$  is

$$\frac{R_2 R_3}{R_2 + R_3}$$

so the total resistance

of this resistor network is  $R_1 + \frac{R_2 R_3}{R_2 + R_3}$

$$= 1k\Omega + \frac{2k \cdot 3k}{5k} \Omega$$

$$= 2.2k\Omega$$

$$V = i R_{eq} \text{ or}$$

$$i = \frac{V}{R_{eq}} = \frac{5V}{2.2k\Omega} = 2.27 \text{ mA out of the battery.}$$

$$i_1 = i = \frac{2.27 \text{ mA}}{1}$$

for  $i_3$  we can use the node rule (KCR)

$$\star \quad i = i_2 + i_3$$

and that  $R_2, R_3$  are parallel so

$$V_2 = V_3$$

$$\star\star \quad i_2 R_2 = i_3 R_3 \Rightarrow i_2 = i_3 \frac{R_3}{R_2}$$

combining  $\star$  and  $\star\star$  gives


$$i = i_3 \frac{R_3}{R_2} + i_3 \Rightarrow i_3 = \frac{i}{1 + R_3/R_2}$$

$$= \frac{2.27 \text{ mA}}{1 + 3/2}$$


$$= \frac{2.27 \text{ mA}}{1.5} = 0.91 \text{ mA}$$

$$\text{and } V_2 = i_2 R_2 = (i - i_3) R_2 = (1.36 \text{ mA}) 2k\Omega = 2.73 \text{ V}$$


2.19 first lets clean up this diagram

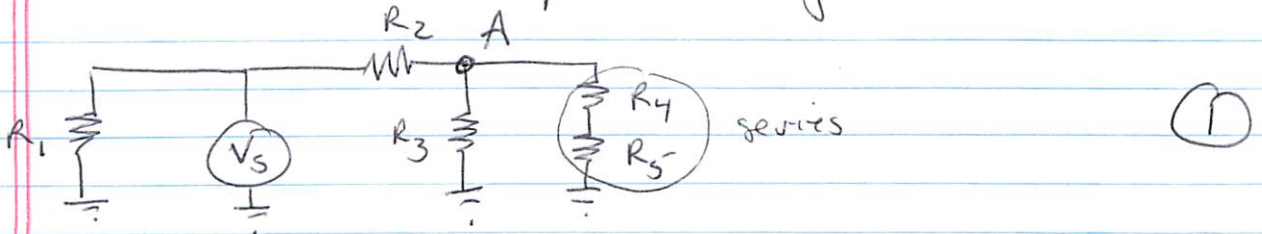


is equivalent to

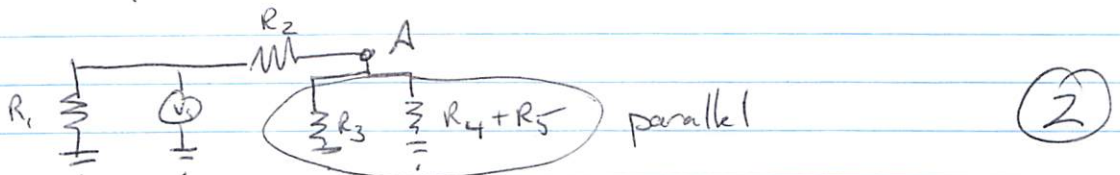


is equivalent to

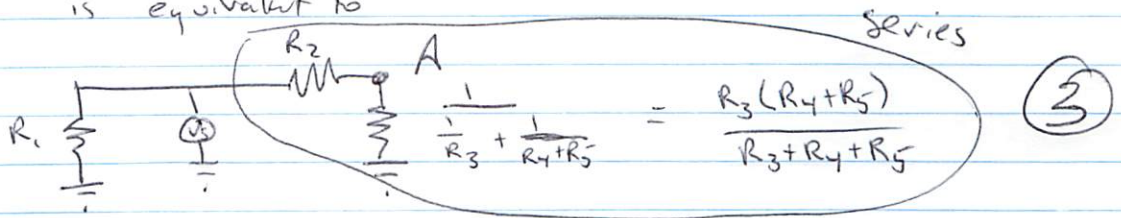

is equivalent to

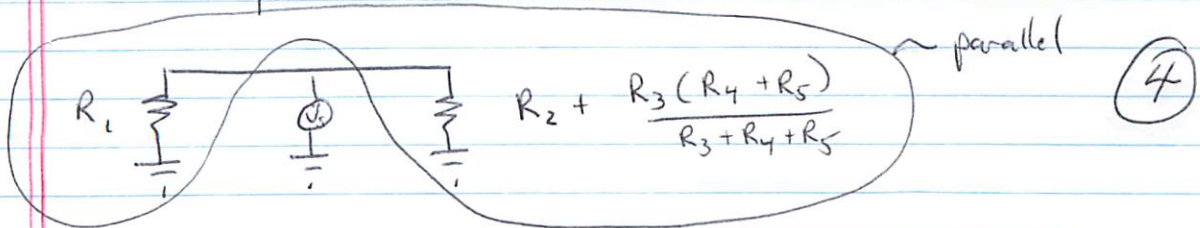

is equivalent to

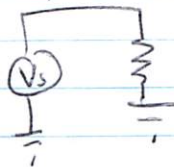

$$R_1 \left( R_2 + \frac{R_3(R_4 + R_5)}{R_3 + R_4 + R_5} \right)$$

$$R_1 + R_2 + \frac{R_3(R_4 + R_5)}{R_3 + R_4 + R_5}$$

and with

$$R_1 = 1k\Omega$$

$$R_2 = 2k\Omega$$


$$R_3 = 3k\Omega$$

$$R_4 = 4k\Omega$$

$$R_5 = 1k\Omega$$

$$R_{eq} = \frac{1k \left( 2k + \frac{3k(5k)}{8k} \right)}{1k + 2k + \frac{3k(5k)}{8k}} = \frac{3.875k}{4.875} = 795\Omega$$

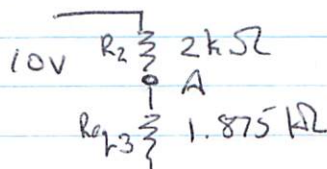looking @ circuit 3 node A is in a voltage divider



so by eq. 2.24  $V_A = \frac{R_2}{R_2 + R_{eq3}} V_s$


$$V_A = \frac{1.875k\Omega}{3.875k\Omega} 10V = 4.8V$$

the voltage across  $R_5$  can be found the same way

$$V_5 = \frac{R_5}{R_4 + R_5} V_A = \frac{1k\Omega}{5k\Omega} 4.8V = 0.97V$$

$$\text{and } V_5 = i_5 R_5 \text{ so } i_5 = \frac{V_5}{R_5} = \frac{0.97V}{1k\Omega} = 0.97mA$$

2.21

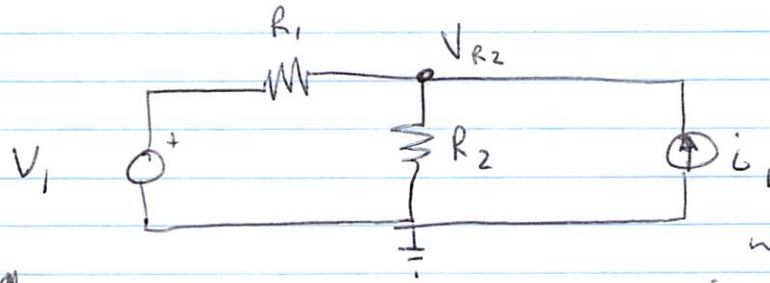

By KVR

$$V_1 - i_{R_1} R_1 - i_{R_2} R_2 = 0$$

and by the node rule (KCL)

$$i_{R_1} + i_1 = i_{R_2}$$

so

$$V_1 - i_{R_1} R_1 - (i_{R_1} + i_1) R_2 = 0$$

$$i_{R_1} (R_1 + R_2) = V_1 - i_1 R_2$$

$$i_{R_1} = \frac{V_1 - i_1 R_2}{R_1 + R_2} \quad \text{and w/ } i_{R_2} = i_{R_1} + i_1$$

we have 
$$i_{R_2} = \frac{i_1 (R_1 + R_2) + V_1 - i_1 R_2}{R_1 + R_2}$$

$$= \frac{i_1 R_1 + V_1}{R_1 + R_2} = \frac{1A \cdot 10\Omega + 1V}{110\Omega}$$

$$= \frac{11V}{110\Omega} = 0.1 \text{ Amps}$$

and 
$$V_{R_2} = i_{R_2} R_2$$
  

$$= 0.1 \text{ Amp} \cdot 100\Omega$$
  

$$= 10V$$

(the rest is going backwards through the battery, charging it.)