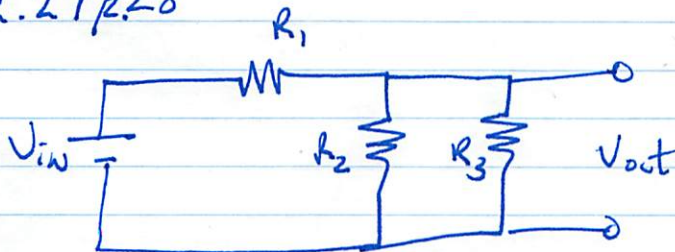


Electronics Homework #2

By hand: 2.27, 2.28

LTspice: 2.20, 2.33

2.27/2.28



We are looking for  $\frac{V_{out}}{V_{in}}$  which is a voltage divider between  $R_1$  ;  $R_{23} = \frac{R_2 R_3}{R_2 + R_3}$

$$\begin{aligned} \text{so} \\ \frac{V_{out}}{V_{in}} &= \frac{R_{23}}{R_1 + R_{23}} = \frac{1}{\frac{R_1}{R_{23}} + 1} \\ &= \frac{1}{\frac{R_1(R_2 + R_3)}{R_2 R_3} + 1} \end{aligned}$$

for resistances a

$$R_1 = 50\Omega, R_2 = 10^4\Omega, R_3 = 10^6\Omega$$

and

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{5 \times 10^1 (10^4 + 10^6)}{10^{10}} + 1} = \frac{1}{1 + 5 \times 10^{-3} (1.01)}$$

$$= 0.995$$

for resistances b  $R_1 = 50\Omega, R_2 = 5 \times 10^5\Omega, R_3 = 10^6\Omega$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{5 \times 10^1 (5 \times 10^5 + 10^6)}{5 \times 10^{11}} + 1} = \frac{1}{1 + 1.5 \times 10^{-4}}$$

$$= 0.9999$$

compared w/ the ideal voltmeter  $R_3 \rightarrow \infty$

and

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{R_1}{R_2} + 1} \quad \text{is a voltage divider.}$$

for resistors a

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{50}{10^4} + 1} = \frac{1}{1 + 5 \times 10^{-3}} = 0.995$$

and resistors b

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{50}{5 \times 10^5} + 1} = \frac{1}{1 + 1 \times 10^{-4}} = 0.9999$$

So if you are truly trying to measure  $\frac{V_{out}}{V_{in}}$  the

difference in both cases is less than a part in  $10^4$ .  
~~and~~ If instead you are trying to get a faithful measure of the voltage across  $R_2$  w/ a real power supply and real voltmeter the power supply has the stronger effect on the reading but they are ~~both~~ all 1 to within 1/2% or better.