

HW#3b

Problem 2.40

$V_{out} = -4.23V$

Power added to circuit:

$P_1 = 121.15mW$

$P_2 = 0.96mW$

$P_3 = -1.92mW$ (battery is being charged).

