


Electronics Chapter 3 homework

3.2, 3.4, 3.15, 3.17, 3.19, 3.20, 3.22, 3.23


3.2 For each circuit determine input signal is

$$V_{in} = 1.0V \sin(2\pi \frac{rad}{s}t) \quad \omega = 2\pi \frac{rad}{s} \Rightarrow T = \frac{2\pi}{\omega} = 1s$$

Amplitude $\frac{\omega}{V} = 1V$

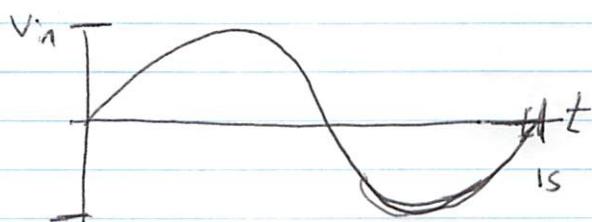

a) V_{out}

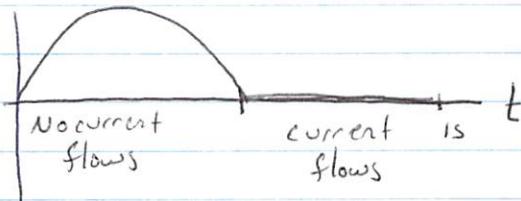

in each case

- the diode supports a voltage drop only if there is no current through it.
- the resistor has a voltage drop only when a current flows through it


b)




c)



d)

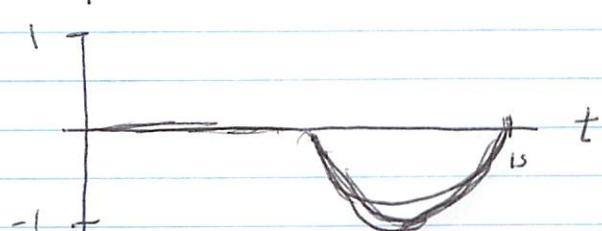


e)

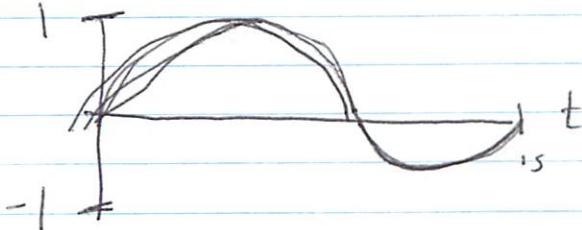

when current flows
the resistors form a
voltage divider.

f)

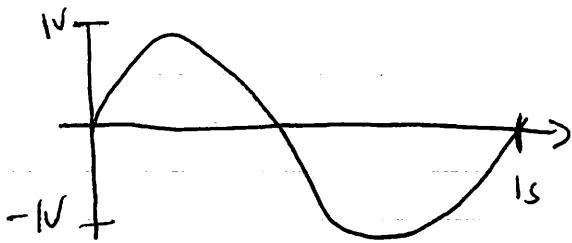



current never flows

3.4 A switch arcs when it opens an inductive load because the sudden change in current causes a large voltage spike by $V = L \frac{di}{dt}$ which is enough to

break down the air between the switch contacts.


The diode provides another path to close the circuit, one that is blocked during normal usage ~~when~~ the switch is closed and only ~~operates~~ when the switch opens and the inductor is dissipating the magnetic ~~energy~~ stored in it.

3.15
a)

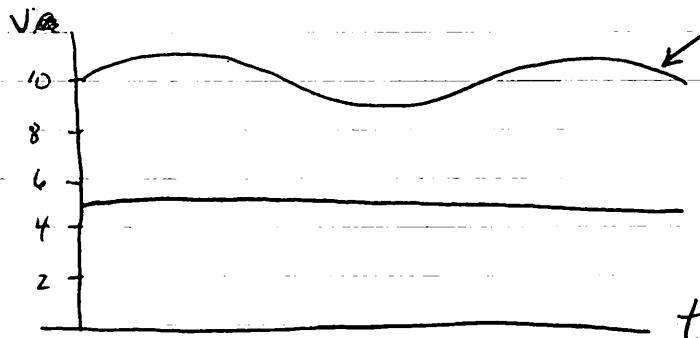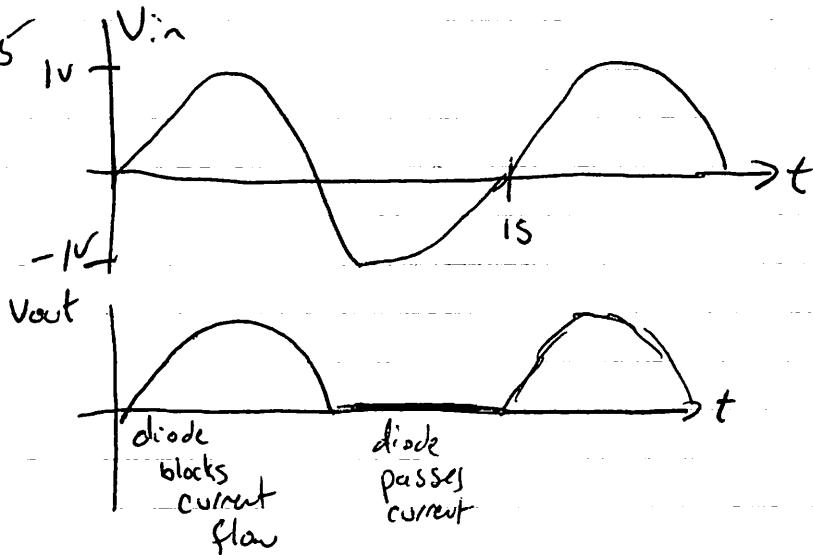

V_{in}
voltage in is consistently
above $V_Z = 5.1V$
so
 $V_{out} = V_Z$

3.17

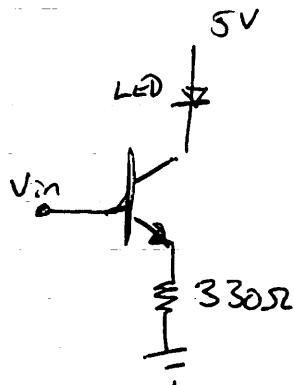

standard value is 0.2V
in saturation mode

$$\text{loop rule } 5V = V_{LED} + V_{CE} + V_R \\ = 2V + 0.2V + V_R$$


$$V_R = 2.8V$$

$$\text{loop rule } V_{in} = V_{be} + V_R \quad \begin{matrix} \text{standard value is 0.7V} \\ \text{in saturation mode.} \end{matrix}$$

$$V_{in} = 0.7V + 2.8V = 3.5V$$

Raising V_{in} will not substantially change the behavior of the circuit.

3.19

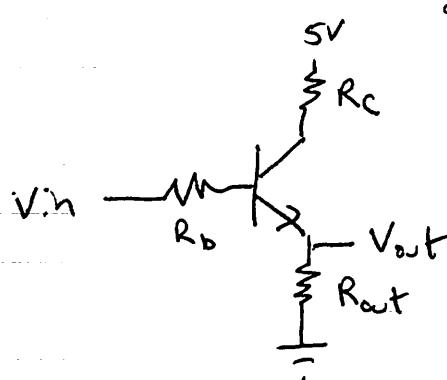

$$\text{loop rule } 5V = V_{RC} + V_{CE} + V_{eot}$$

$$= i_C R_C + 0.2V + i_e R_{out}$$

$$\text{loop rule } V_{in} = V_{RB} + V_{BE} + V_{Rout}$$

$$= i_B R_B + 0.7 + i_C R_{out}$$

node rule $i_e = i_b + i_c$ and $i_c = i_b \beta$

this implies $i_e = (1+\beta) i_b$
so

$$\star V_{in} = i_b R_B + 0.7V + (1+\beta) R_{out} i_b$$

$$= 0.7V + (R_B + R_{out} + \beta R_{out}) i_b$$

and


$$5V = \beta i_b R_C + 0.2V + (1+\beta) i_b R_{out}$$

$$i_b = \frac{4.8V}{(R_{out} + \beta(R_C + R_{out}))} = \frac{4.8V}{201k\Omega} = 0.024mA$$

from \star

$$V_{in} = 0.7V + (102k\Omega) i_b \\ = 3.14V$$

3.20

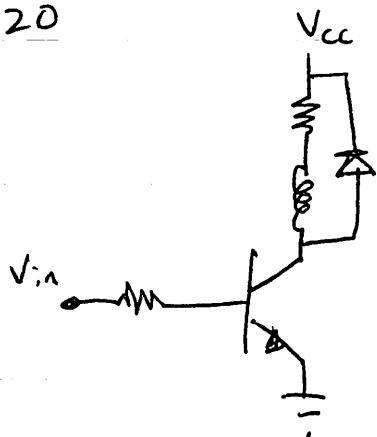

24V when on.

$$\text{In saturation } V_{CE} = 0.2V$$

$$\text{so } V_{CC} = 24V + 0.2V = 24.2V$$

if we assume $\beta = 100$ then

$$i_B = \frac{1A}{\beta} = \frac{1A}{100} = 10mA$$

$$V_{in} = i_B R_b + V_{BE}$$

when on

$$5V = 10mA R_b + 0.7V$$

and

$$R_b = \frac{4.3V}{10mA} = 430\Omega$$

3.22 in the fully on state, from graph


$$V_{ds} = 0.2V$$

$$i_{ds} = 48mA$$

and

$$V_{ds} = i_{ds} R_{on} \Rightarrow R_{on} = \frac{0.2V}{0.048A} = 4.2\Omega$$

3.23

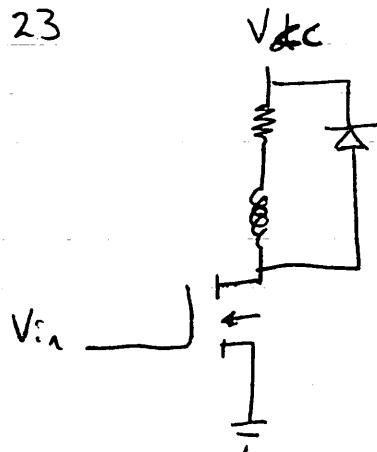

No gate resistor
needed.